

Physics Year 11

Electrical Circuits

Voltmeters & Ammeters


- Voltmeter –measures PD between 2 points
- Connected in parallel to the component it is measuring the PD across
- High resistance instruments (little I diverted)
- Ammeter measures I at a point
- Connected in series
- Very low resistance (little effect on I)
- Polarities – right way round

Series Circuits

- Resistors connected end to end = series
- Resistors connected in series V is shared among resistors
- $V = V_1 + V_2 + V_3$
- Same I goes through all
- Total resistance is the sum of the individuals

Worked Example

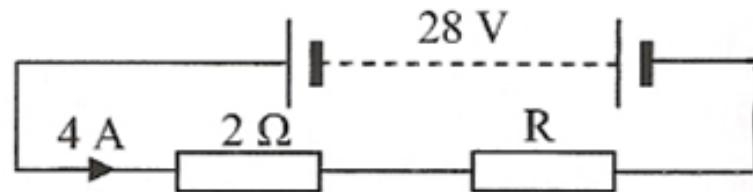A $2\ \Omega$ resistor is connected in series with an unknown resistor R and a battery supplying $28\ \text{V}$. The current in the circuit was measured at $4\ \text{A}$. Calculate



a) *The value of R*

$$\text{Total resistance} = V/I = 28/4 = 7\ \Omega \quad \text{so } R = 5\ \Omega$$

b) *The voltages across each of the two resistors*

$$V_1 = IR_1 = 4 \times 2 = 8\ \text{V}$$


$$V_2 = IR_2 = 4 \times 5 = 20\ \text{V}$$

Disadvantages of Series Circuits

- Series circuits have two disadvantages when compared with parallel circuits.
- The first disadvantage is that, if one component in a series circuit fails, then all the components in the circuit fail because the circuit has been broken.
- The second disadvantage is that the more components there are in a series circuit, the greater the circuit's resistance.

Parallel Circuits

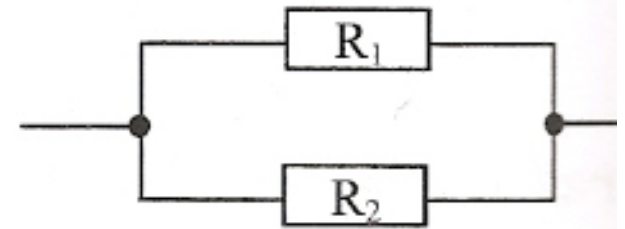
- In parallel means placing it by the side of another
- If R_1 is connected as




- Then amount of I flowing in the circuit increases
- Reason = R_2 allows I to flow in another pathway
- I is shared among resistors
- Same V across each
- Total resistance is less than

Parallel Circuits continued

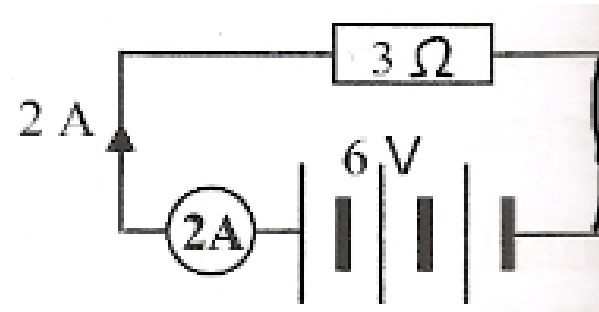- 3 ohm resistor & 6 V cell
- $I \text{ flowing} = 6/3 = 2\text{A}$




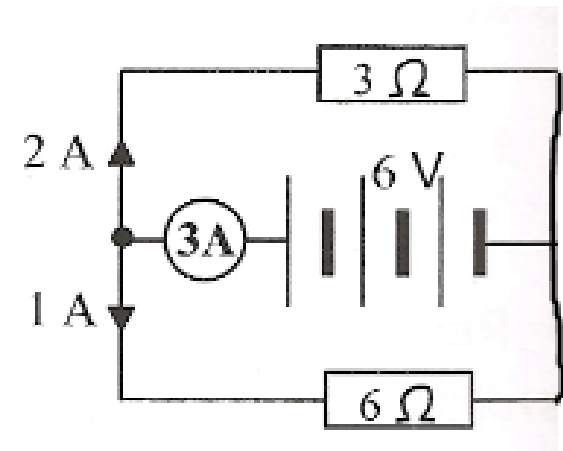- Another resistor of 6 ohms
- Forms separate circuit
- $I = 6/6 = 1\text{A}$
- Total I flowing from cell = $2+1\text{A}$
- Total $R = V/I = 6/3 = 2$ ohms



Rules for a Parallel Circuit.

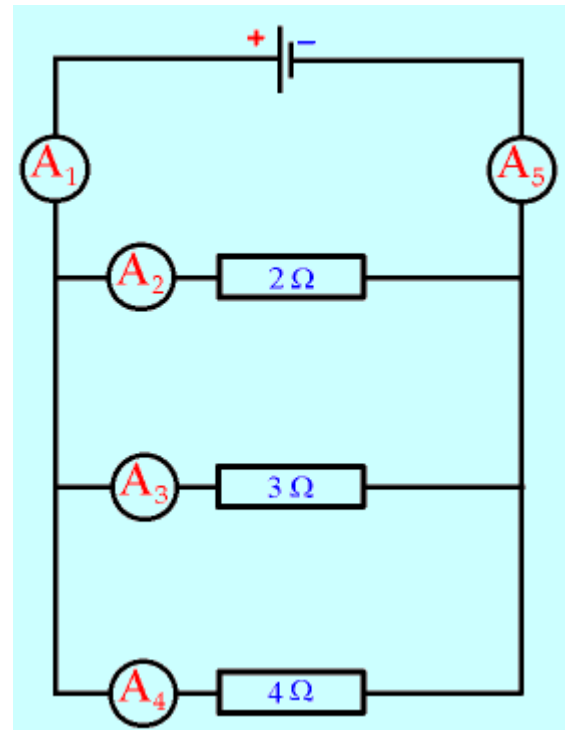- Current in a Parallel Circuit.
- The current in a parallel circuit depends on the resistance of the branch.
- The total current flowing in to the branches is equal to the total current flowing out of the branches.
- $A_1 = A_5$



Current in a Parallel Circuit.


- The current at A2 flowing through the 2 Ohm resistor can be found using $V = I \times R$

- If the supply voltage is 12 Volt

- $I = V / R$

- $= 12 / 2$

- $= 6 \text{ Amps.}$

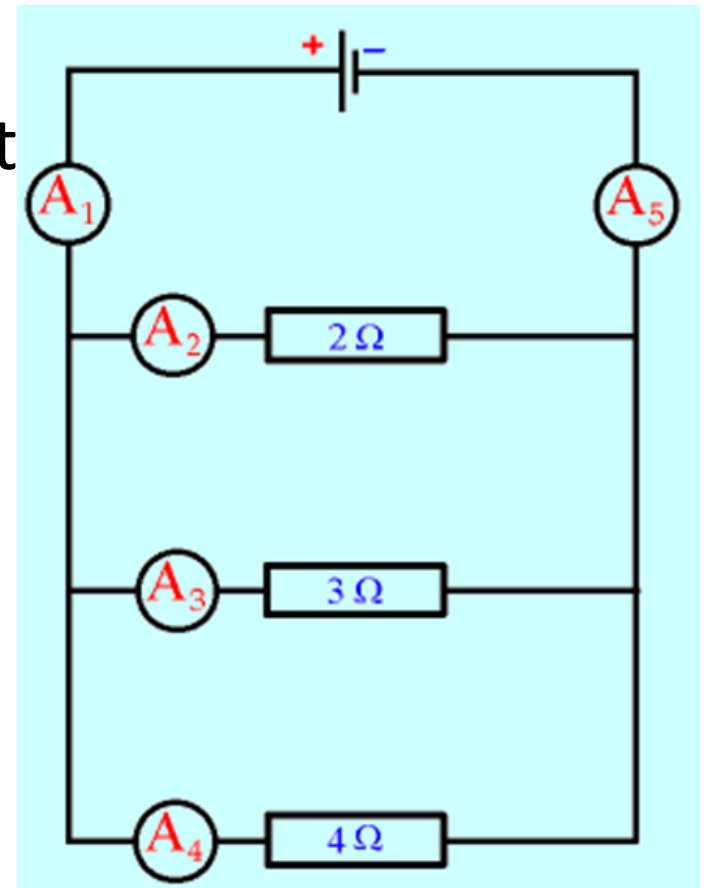


Parallel Notes

- For parallel circuits, each component behaves as if it is connected independently to the cell, and is unaware of the other components
- If an identical cell (battery) is placed in parallel with the original cell the current stays the same because the total voltage of the circuit is the same.
- The two cells together provide electricity for twice as long before they both run out.


Current in a Parallel Circuit (continued).

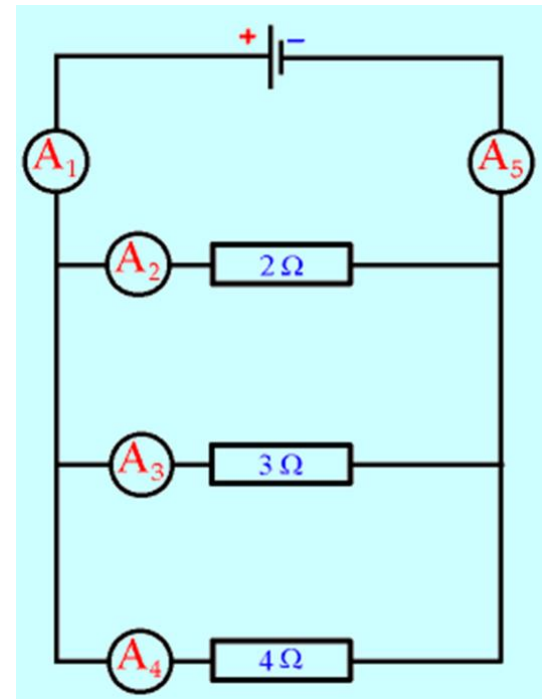- The current A_2 flowing through the 2 Ohm resistor is 6 Amps.
- The current A_3 flowing through the 3 Ohm resistor is
- $I = V / R$
- $= 12 / 3$
- $= 4$ Amps.
- The current A_4 flowing through
- the 4 Ohm resistor is
- $I = V / R = 12 / 4$
- $= 3$ Amps.
- Notice that the bigger the resistance, the smaller the current.




Current in a Parallel Circuit (continued)

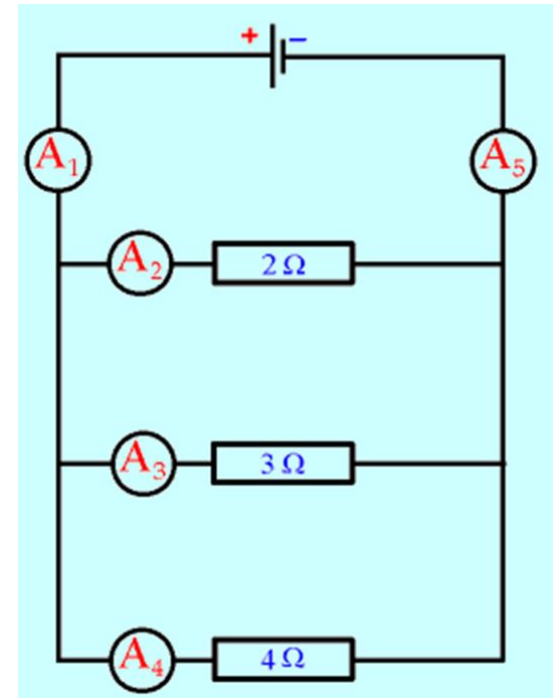- The total current A_1 or A_5 is found by adding up the current in each branch.
- $A_1 = A_2 + A_3 + A_4$
- $= 6 + 4 + 3$
- $= 13$ Amps.
- This is much larger than the current of 1.333 Amps which flows through a series circuit with the same resistors and supply voltage



Voltage in a Parallel Circuit.

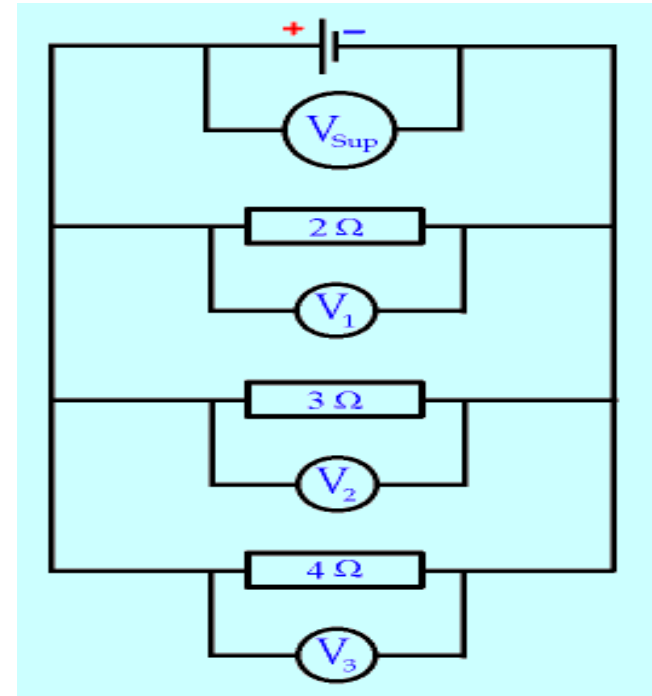- The voltage in a parallel circuit is the same for all branches.
- $V_1 = V_2 = V_3$.
- The voltage for each branch is the same as the supply voltage.
- $V_1 = V_2 = V_3 = V_{\text{sup}}$.



- If an identical cell (battery) is placed in parallel with the original cell the voltage stays the same.
- The two cells together provide electricity for twice as long before they run out.


Resistance in a Parallel Circuit.

- The total resistance of a parallel circuit is calculated using the formula
- $1/R = 1/R_1 + 1/R_2 + 1/R_3 \dots$

Worked Example

- $1/R = 1/2 + 1/3 + 1/4$
- $= 6/12 + 4/12 + 3/12$
- $= 13/12$
-
- (You want R not 1/R so flip both
- Sides of the equal sign to give you R)

- $R = 12/13$
- $= 0.92 \text{ Ohms.}$

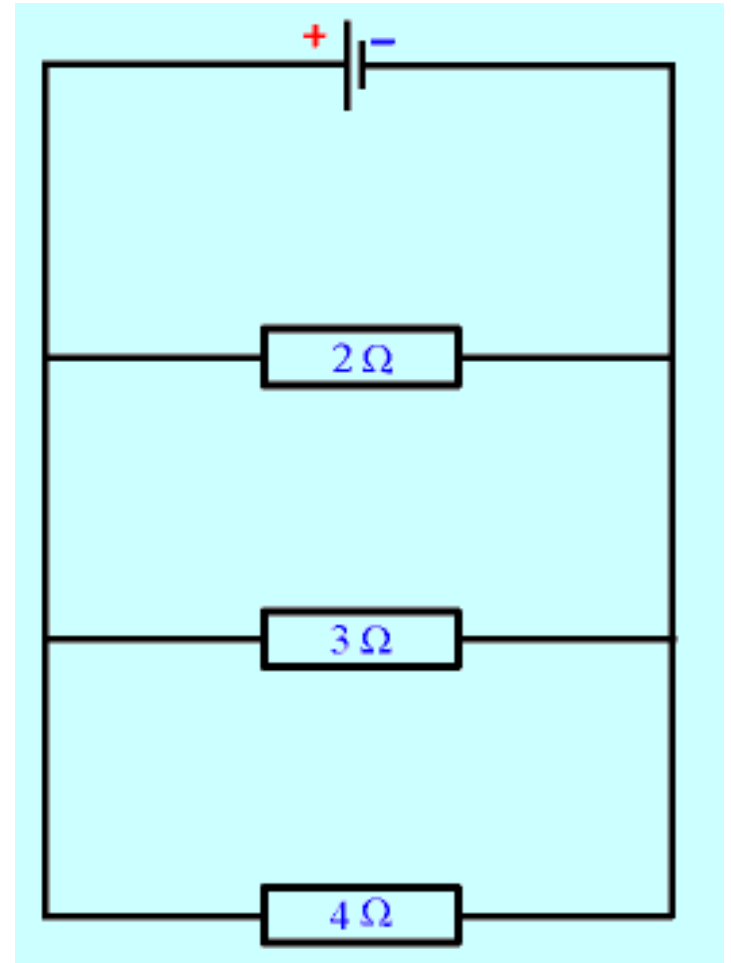

Parallel Resistance Notes

- Notice that this is a much smaller resistance than you get in the series circuit using the same resistors.
- It is even smaller than the smallest resistor in the parallel circuit, which is 2 Ohms.
- Putting more resistors in the parallel circuit decreases the total resistance because the electricity has additional branches to flow along and so the total current flowing increases.