

# Physics Year 11

## Electrical Circuits

# Voltmeters & Ammeters


- Voltmeter –measures PD between 2 points
- Connected in parallel to the component it is measuring the PD across
- High resistance instruments (little  $I$  diverted)
- Ammeter measures  $I$  at a point
- Connected in series
- Very low resistance (little effect on  $I$ )
- Polarities – right way round

# Series Circuits

- Resistors connected end to end = series
- Resistors connected in series  $V$  is shared among resistors
- $V = V_1 + V_2 + V_3$
- Same  $I$  goes through all
- Total resistance is the sum of the individuals
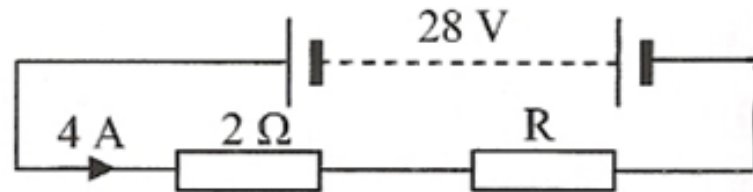
# Worked Example

*A  $2\ \Omega$  resistor is connected in series with an unknown resistor  $R$  and a battery supplying  $28\ \text{V}$ . The current in the circuit was measured at  $4\ \text{A}$ . Calculate*



a) *The value of  $R$*

$$\text{Total resistance} = V/I = 28/4 = 7\ \Omega \quad \text{so } R = 5\ \Omega$$

b) *The voltages across each of the two resistors*

$$V_1 = IR_1 = 4 \times 2 = 8\ \text{V}$$


$$V_2 = IR_2 = 4 \times 5 = 20\ \text{V}$$

# Disadvantages of Series Circuits

- Series circuits have two disadvantages when compared with parallel circuits.
- The first disadvantage is that, if one component in a series circuit fails, then all the components in the circuit fail because the circuit has been broken.
- The second disadvantage is that the more components there are in a series circuit, the greater the circuit's resistance.
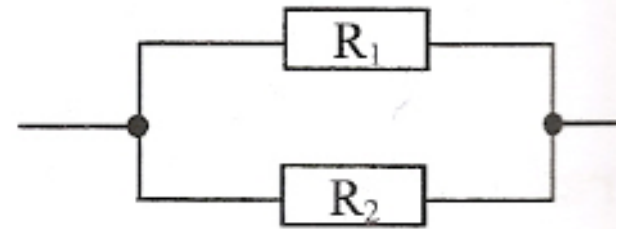
# Parallel Circuits


- In parallel means placing it by the side of another
- If  $R_1$  is connected as




- Then amount of  $I$  flowing in the circuit increases
- Reason =  $R_2$  allows  $I$  to flow in another pathway
- $I$  is shared among resistors
- Same  $V$  across each
- Total resistance is less than
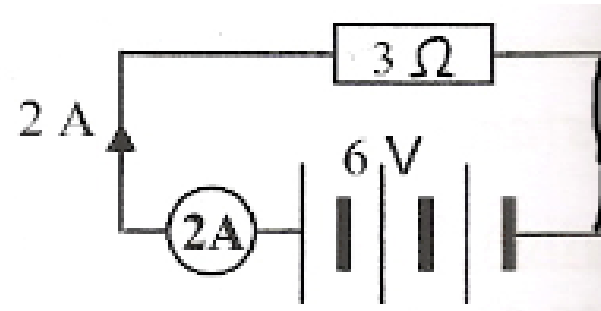
# Parallel Circuits continued

- 3 ohm resistor & 6 V cell
- $I \text{ flowing} = 6/3 = 2\text{A}$




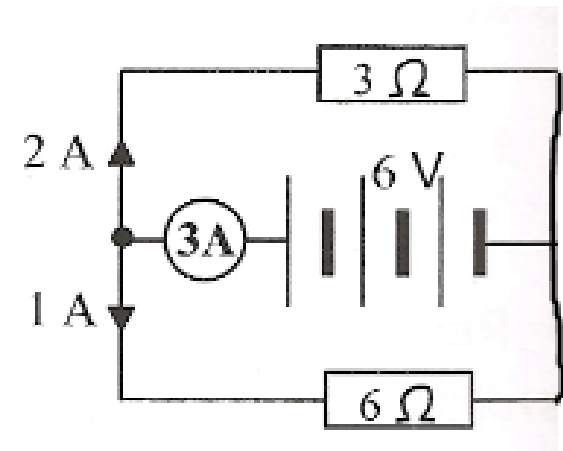- Another resistor of 6 ohms
- Forms separate circuit
- $I = 6/6 = 1\text{A}$
- Total  $I$  flowing from cell =  $2+1\text{A}$
- Total  $R = V/I = 6/3 = 2$  ohms


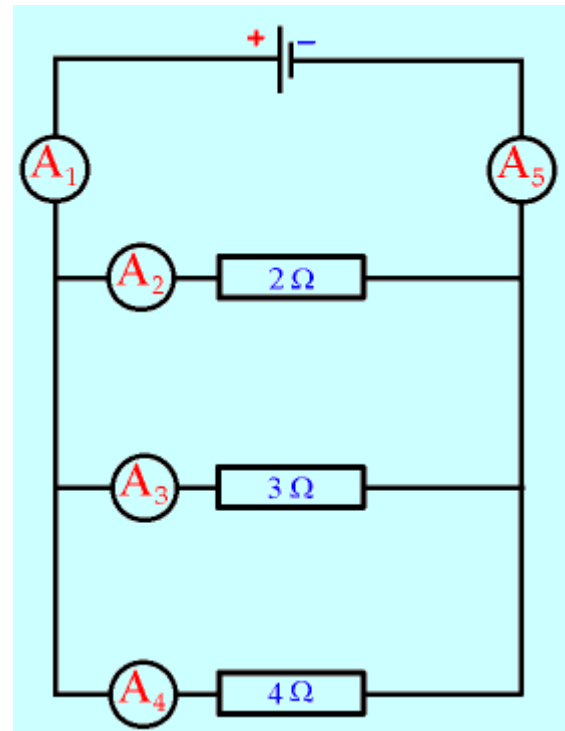
## Rules for a Parallel Circuit.

- Current in a Parallel Circuit.
- The current in a parallel circuit depends on the resistance of the branch.
- The total current flowing in to the branches is equal to the total current flowing out of the branches.
- $A_1 = A_5$



# Current in a Parallel Circuit.


- The current at A2 flowing through the 2 Ohm resistor can be found using  $V = I \times R$

- If the supply voltage is 12 Volt

- $I = V / R$

- $= 12 / 2$

- $= 6 \text{ Amps.}$

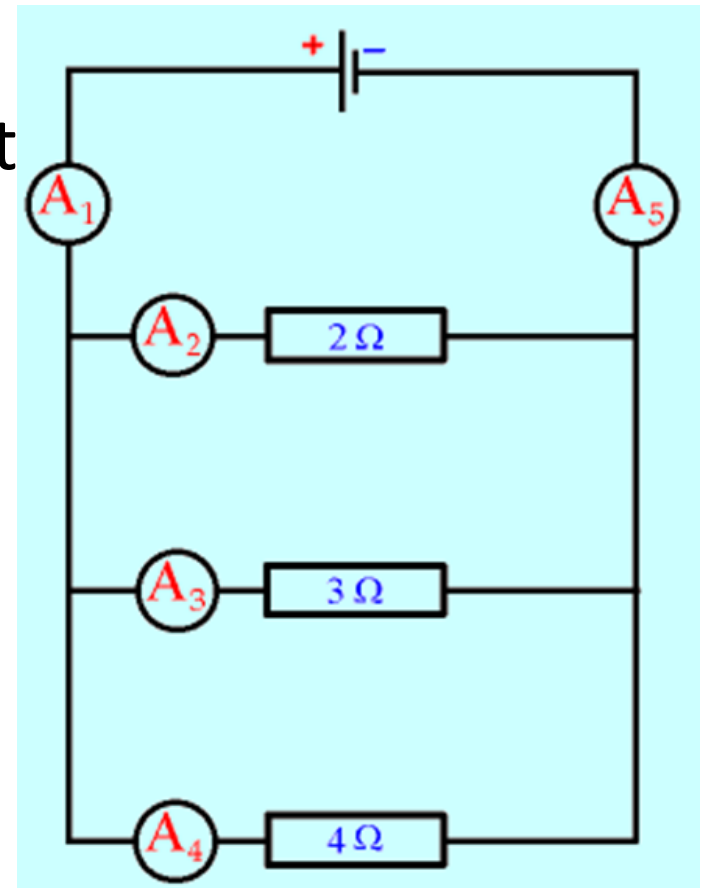


# Parallel Notes

- For parallel circuits, each component behaves as if it is connected independently to the cell, and is unaware of the other components
- If an identical cell (battery) is placed in parallel with the original cell the current stays the same because the total voltage of the circuit is the same.
- The two cells together provide electricity for twice as long before they both run out.

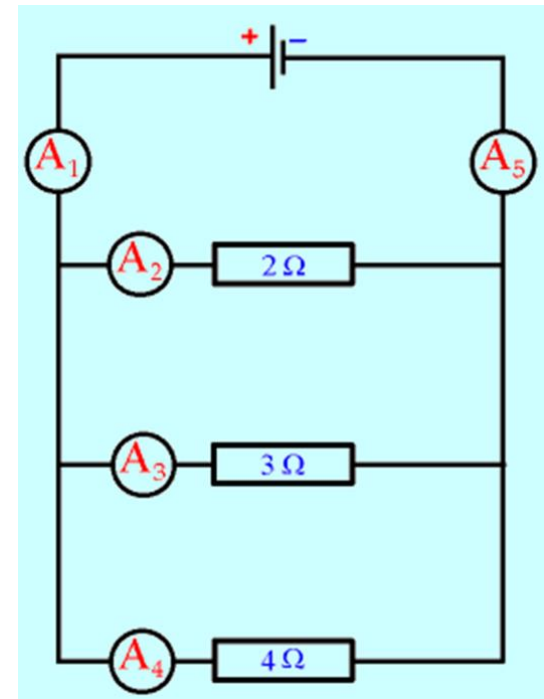
## Current in a Parallel Circuit (continued).

- The current  $A_2$  flowing through the 2 Ohm resistor is 6 Amps.
- The current  $A_3$  flowing through the 3 Ohm resistor is
- $I = V / R$
- $= 12 / 3$
- $= 4$  Amps.
- The current  $A_4$  flowing through
- the 4 Ohm resistor is
- $I = V / R = 12 / 4$
- $= 3$  Amps.
- Notice that the bigger the resistance, the smaller the current.



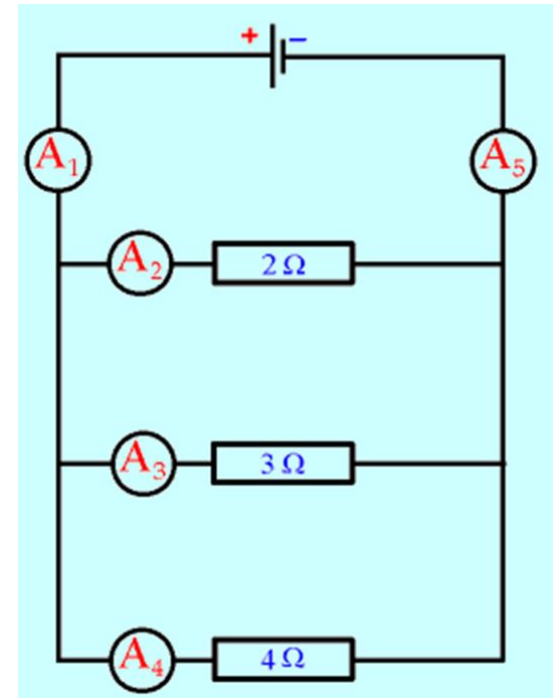
# Current in a Parallel Circuit (continued)

- The total current  $A_1$  or  $A_5$  is found by adding up the current in each branch.
- $A_1 = A_2 + A_3 + A_4$
- $= 6 + 4 + 3$
- $= 13$  Amps.
- This is much larger than the current of 1.333 Amps which flows through a series circuit with the same resistors and supply voltage


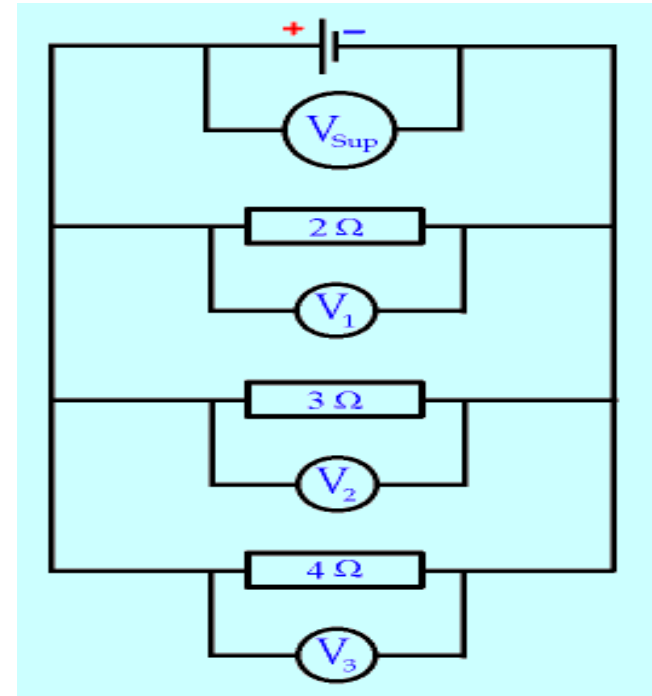
# Voltage in a Parallel Circuit.

- The voltage in a parallel circuit is the same for all branches.
- $V_1 = V_2 = V_3$ .
- The voltage for each branch is the same as the supply voltage.
- $V_1 = V_2 = V_3 = V_{\text{sup}}$ .




- If an identical cell (battery) is placed in parallel with the original cell the voltage stays the same.
- The two cells together provide electricity for twice as long before they run out.

# Resistance in a Parallel Circuit.

- The total resistance of a parallel circuit is calculated using the formula
- $1/R = 1/R_1 + 1/R_2 + 1/R_3 \dots$
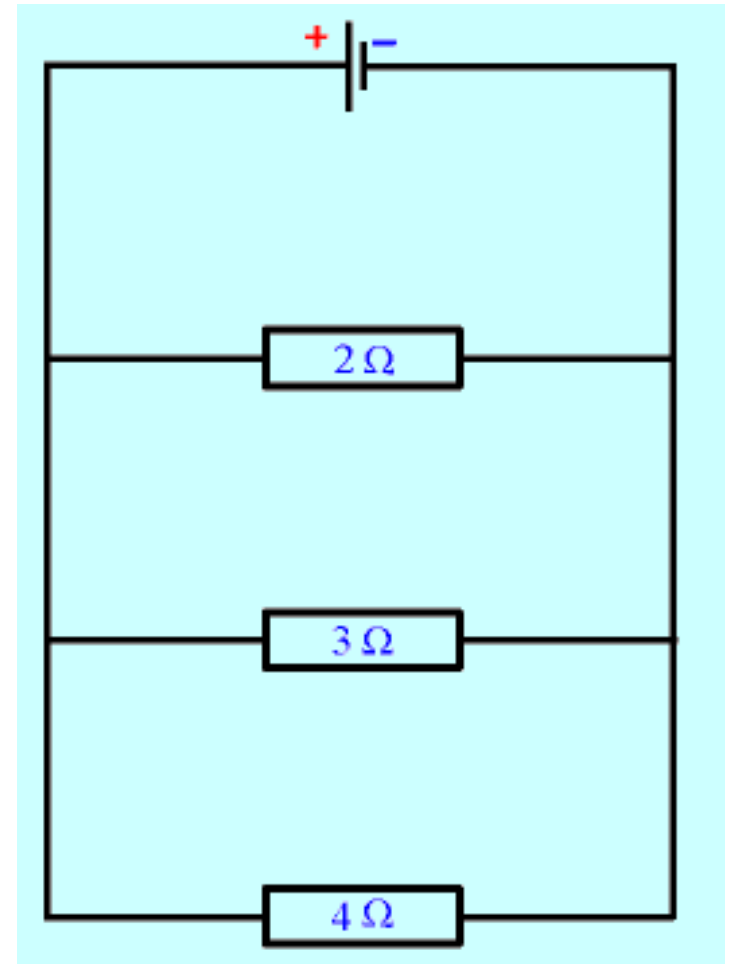
# Worked Example

- $1/R = 1/2 + 1/3 + 1/4$
- $= 6/12 + 4/12 + 3/12$
- $= 13/12$
- $R = 12/13$
- $= 0.92 \text{ Ohms.}$



# Parallel Resistance Notes

- Notice that this is a much smaller resistance than you get in the series circuit using the same resistors.
- It is even smaller than the smallest resistor in the parallel circuit, which is 2 Ohms.
- Putting more resistors in the parallel circuit decreases the total resistance because the electricity has additional branches to flow along and so the total current flowing increases.