

# PQ 11

Questions and Answers

# Q1

A 110-volt toaster oven draws a current of 6 amps on its highest setting as it converts electrical energy into thermal energy. What is the toaster's maximum power rating?

$$P = VI = (110V)(6A) = 660W$$

## Q2

An electric iron operating at 120 volts draws 10 amperes of current. How much heat energy is delivered by the iron in 30 seconds?

$$W = Pt = VI t = (120V)(10A)(30s) = 3.6 \times 10^4 J$$

# Q3

One watt is equivalent to one

... J/s, since Power is  $W/t$ , and the unit of work is the joule, and the unit of time is the second.

# Q4

A potential drop of 50 volts is measured across a 250-ohm resistor. What is the power developed in the resistor?

$$P = \frac{V^2}{R} = \frac{(50V)^2}{250\Omega} = 10W$$

# Q5

A driving lamp fitted to a car is specified as a 100 W, 12.0 V lamp.  
Calculate

- (a) the current flowing through the lamp, and
- (b) the resistance of the lamp.

$$\begin{aligned}(a) \quad P &= VI \\ 100 &= 12.0 I \\ \therefore I &= 8.33 A\end{aligned}$$

$$\begin{aligned}(b) \quad V &= IR \\ 12.0 &= 8.33 R \\ \therefore R &= 1.44 \Omega\end{aligned}$$

# Q6

An electric motor found in a child's toy requires two 1.50 V dry cell batteries to be connected in series. If the motor draws a maximum current of 300 mA calculate

- (a) the resistance of the motor, and
- (b) the maximum power consumption of the toy.

$$\begin{aligned}(a) \quad V &= IR \\ 3.00 &= 0.300 R \\ \therefore R &= 10.0 \Omega\end{aligned}$$

$$\begin{aligned}(b) \quad P &= VI \\ &= 3.00 \times 0.300 \\ \therefore P &= 0.900 W\end{aligned}$$

# Q7

A Christmas tree is decorated by a string of 16 light globes which are connected in series to a mains outlet of 240 V. If the total power consumption is 24.0 W, calculate the

- (a) potential difference across each light globe, and
- (b) resistance of each light globe.

$$(a) \quad \begin{aligned} & \text{Potential difference across each globe} \\ &= \frac{240}{16} = 15 \text{ V} \end{aligned}$$

$$(b) \quad \text{Power} = \frac{V^2}{R}$$

$$R = \frac{(240)^2}{24} = 2.40 \times 10^3 \Omega$$

$$\text{Resistance of circuit} = 2.40 \times 10^3 \Omega$$

$$\therefore \text{Resistance of each globe} = \frac{2.40 \times 10^3}{16}$$

$$= 150 \Omega$$

# Q8

Charles wishes to connect a number of 75.0 W, 240 V coloured party light globes around his patio. How many globes can he use without blowing a 10.0 A fuse when he turns the light globes on?

$$\text{Maximum power output} = VI$$

$$= 240 \times 10$$

$$= 2400 \text{ W}$$

$\therefore$  Number of 75 W light globes

$$\text{which would blow the fuse} = \frac{2400}{75}$$

$$= 32$$


$\therefore$  Maximum number of light globes to be used

$$= 31$$

# Q9

For the circuit drawn below calculate the

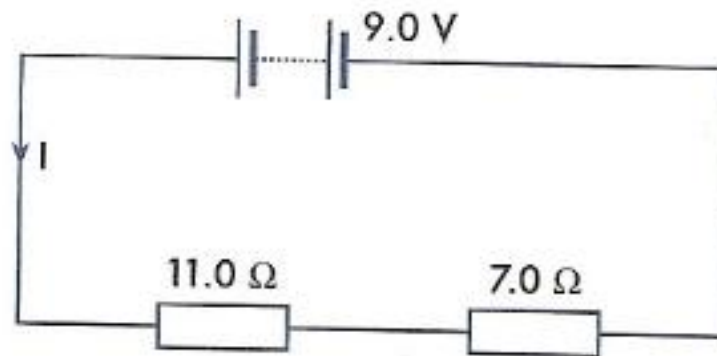- (a) total resistance of the circuit, and
- (b) the current,  $I$ .



$$\begin{aligned}(a) \quad R_T &= R_1 + R_2 \\ &= 11 + 7 \\ &= 18 \Omega\end{aligned}$$

$\therefore$  Resistance of circuit =  $18 \Omega$


$$\begin{aligned}(b) \quad V &= IR \\ 9.0 &= I \times 18 \\ \therefore I &= 0.50 A\end{aligned}$$

$\therefore$  Current through circuit =  $0.50 A$

# Q10

For the circuit drawn below calculate the

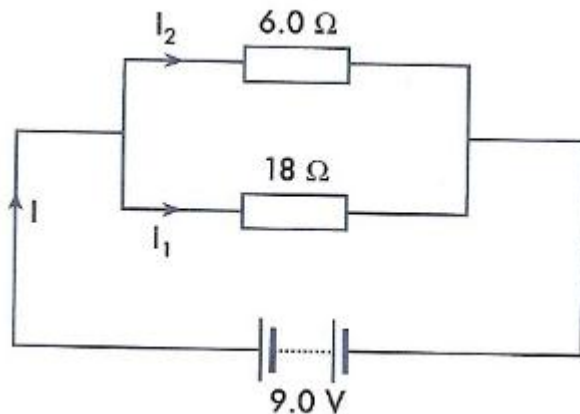- (a) total resistance of the circuit,
- (b)  $I$ ,
- (c)  $I_1$ , and
- (d) the potential difference across the  $6.0 \Omega$  resistor.



$$\begin{aligned}(a) \quad \frac{1}{R_T} &= \frac{1}{R_1} + \frac{1}{R_2} \\ &= \frac{1}{18} + \frac{1}{6} \\ &= \frac{1+3}{18} \\ &= \frac{4}{18}\end{aligned}$$

$$\therefore R_T = 4.5 \Omega$$

$$\therefore \text{Resistance of circuit} = 4.5 A$$

$$\begin{aligned}(b) \quad V &= IR \\ 9.0 &= I \times 4.5 \\ \therefore I &= 2.0 A\end{aligned}$$

$$\begin{aligned}(c) \quad I_1 &= \frac{9.0}{1.8} \\ &= 0.5 A\end{aligned}$$

$$\begin{aligned}(d) \quad I &= I_1 + I_2 \\ 2.0 &= 0.5 + I_2 \\ \therefore I_2 &= 1.5 A \\ \therefore PD &= IR \\ &= 1.5 \times 6.0 \\ &= 9.0 V\end{aligned}$$