


# PQ 12

Questions and Answers

# Q1

For the circuit drawn below calculate the

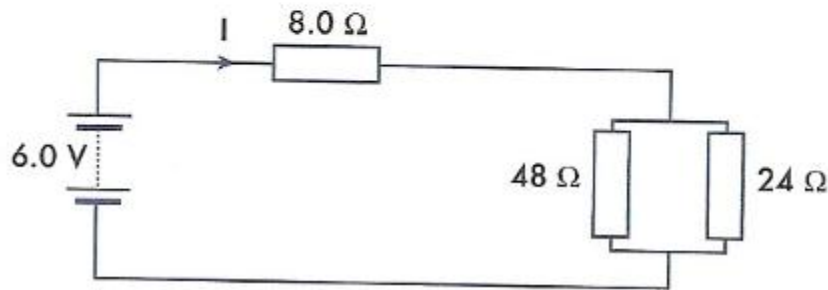- (a) total resistance of the circuit,
- (b)  $I$ ,
- (c) potential difference across the  $24\ \Omega$  resistor, and
- (d) power dissipated through  $8.0\ \Omega$  resistor.



(a) In parallel section: 
$$\frac{1}{R_T} = \frac{1}{48} + \frac{1}{24}$$
$$= \frac{1+2}{48} = \frac{3}{48}$$

$$\therefore R_T = 16\ \Omega$$

$$\therefore \text{Total resistance of circuit} = 8.0 + 16$$
$$= 24\ \Omega$$

(b)  $V = IR$   
 $6.0 = I \times 24$   
 $\therefore I = 0.25\ A$

(c) P.D. across parallel section =  $IR_T$   
 $= 0.25 \times 16$   
 $= 4.0\ V$   
 $\therefore$  P.D. across  $24\ \Omega$  resistor =  $4.0\ V$

(d)  $P = I^2 R$   
 $= (0.25)^2 \times 8.0$   
 $= 0.50\ W$   
 $\therefore$  Power dissipated through  $8.0\ \Omega$  resistor =  $0.50\ W$

## Q2

Kylie made a cup of coffee by boiling 300 mL of water in an electric kettle which had the following written on its base: 240 V, 2400 W

If the kettle took 50.0 seconds to boil the water,

- (a) how much electrical energy was used in this time, and
- (b) can Kylie expect all of the heat energy transformed from this electrical energy to be absorbed by the water in the kettle and heat it to boiling point?

$$\begin{aligned}(a) \text{ Electrical energy supplied} &= P \times t \\ &= 2400 \times 50.0 = 1.20 \times 10^5 \text{ J}\end{aligned}$$

(b) No. Some of the internal energy transformed from the electrical energy in the kettle will be used to heat the kettle and escape to the surroundings.

# Q3

A television set owned by Michael is rated at 180 W and is designed to operate on a 240 V supply. If standard values for fuses are 2.00 A, 5.00 A and 10.0 A,

- (a) suggest a value for a fuse to be placed in the circuit to which Michael's television is connected, and
- (b) if a 10.0 A fuse was inadvertently used instead of the recommended fuse, predict what may happen if fault in the television caused a much larger current to flow in the television set.

$$(a) P = VI$$

$$180 = 240 I$$

$$\therefore I = 0.75 A$$

$\therefore$  Use a 2.00 A fuse.

(b) *Components in the television set may be damaged by the excessive current or a fire may start in the television set before the 10.0 A fuse is made to 'blow' by this larger current.*

# Q4

List three advantages of using an earth leakage circuit breaker.

- (i) switch off an electric current in a very short time,*
- (ii) quickly stop an electric shock or reduce the chances of an electrocution occurring,*
- (iii) prevent a fire occurring in an electrical appliance due to a fault causing a current to flow through earth wires.*

# Q5

The 12.0 V battery in a car supplies a current of  $3.50 \times 10^2$  A to provide the starter motor with maximum power.

- Calculate the maximum power of the starter motor.
- Determine the maximum resistance of the starter motor, the battery and the connective wires.
- Compare the thickness of the wire connecting the battery to the starter motor with the thickness of the wire used in most other circuits in the car. Give a reason for your answer.

$$(a) P = VI = 12.0 \times 3.50 \times 10^2 = 4.20 \times 10^3 \text{ W}$$

$$(b) R = \frac{V}{I} = \frac{12.0}{3.50 \times 10^2} = 3.43 \times 10^{-2} \Omega$$

*(c) The battery to starter motor wire is much thicker for it to have a small resistance (less than  $3.43 \times 10^{-2} \Omega$ ) and to carry a very large current.*