

PQ 13 Electricity

Q and A

Q1

- The current through a globe connected across the terminals of a 125-V outlet is 0.50 A. At what rate does the bulb convert electric energy to light?

$$P = IV = (0.50 \text{ A})(125 \text{ V}) = 63 \text{ J/s} = 63 \text{ W}$$

Q2

- A van battery causes a current of 2.0 A through a lamp and produces 12 V across it. What is the power used by the lamp?

$$P = IV = (2.0 \text{ A})(12 \text{ V}) = 24 \text{ W}$$

Q3

- What is the current through a 75-W globe that is connected to a 125-V outlet?

$$P = IV$$

$$I = \frac{P}{V} = \frac{75 \text{ W}}{125 \text{ V}} = 0.60 \text{ A}$$

Q4

- The current through the starter motor of a van is 210 A. If the battery maintains 12 V across the motor, how much electric energy is delivered to the starter in 10.0 s?

$$P = IV \text{ and } E = Pt$$

$$\begin{aligned} \text{Thus, } E &= IVt = (210 \text{ A})(12 \text{ V})(10.0 \text{ s}) \\ &= 2.5 \times 10^4 \text{ J} \end{aligned}$$

Q5

- A torch bulb is rated at 0.90 W. If the light bulb drops 3.0 V, how much current goes through it?

$$P = IV$$

$$I = \frac{P}{V} = \frac{0.90 \text{ W}}{3.0 \text{ V}} = 0.30 \text{ A}$$

Q6

- An automobile panel lamp with a resistance of 33 ohm's is placed across a 12-V battery. What is the current through the circuit?

$$I = \frac{V}{R} = \frac{12 \text{ V}}{33 \ \Omega} = 0.36 \text{ A}$$

Q7

- A lamp draws a current of 0.50 A when it is connected to a 120-V source.
- **a.** What is the resistance of the lamp?

$$R = \frac{V}{I} = \frac{120 \text{ V}}{0.50 \text{ A}} = 2.4 \times 10^2 \Omega$$

- **b.** What is the power consumption of the lamp?

$$P = IV = (0.50 \text{ A})(120 \text{ V}) = 6.0 \times 10^1 \text{ W}$$

Q8

- A 75-W lamp is connected to 125 V.
- **a.** What is the current through the lamp?

$$I = \frac{P}{V} = \frac{75 \text{ W}}{125 \text{ V}} = 0.60 \text{ A}$$

- **b.** What is the resistance of the lamp?

$$R = \frac{V}{I} = \frac{125 \text{ V}}{0.60 \text{ A}} = 2.1 \times 10^2 \text{ } \Omega$$

Q9

- A resistor is added to the lamp in the previous problem to reduce the current to half of its original value.
- a. What is the potential difference across the lamp?

The new value of the current is

$$\frac{0.60 \text{ A}}{2} = 0.30 \text{ A}$$

$$\begin{aligned} V &= IR = (0.30 \text{ A})(2.1 \times 10^2 \Omega) \\ &= 6.3 \times 10^1 \text{ V} \end{aligned}$$

Q9 continued

- **b.** How much resistance was added to the circuit?

The total resistance of the circuit is now

$$R_{\text{total}} = \frac{V}{I} = \frac{125 \text{ V}}{0.30 \text{ A}} = 4.2 \times 10^2 \Omega$$

Therefore,

$$\begin{aligned} R_{\text{res}} &= R_{\text{total}} - R_{\text{lamp}} \\ &= 4.2 \times 10^2 \Omega - 2.1 \times 10^2 \Omega \\ &= 2.1 \times 10^2 \Omega \end{aligned}$$

- **c.** How much power is now dissipated in the lamp?

$$P = IV = (0.30 \text{ A})(6.3 \times 10^1 \text{ V}) = 19 \text{ W}$$

Q10

- A 100W light bulb is 22 percent efficient.
- **a.** How many joules does the light bulb convert into light each minute it is in operation?

$$\begin{aligned} E &= Pt \\ &= (0.22)(100.0 \text{ J/s})(1.0 \text{ min}) \\ &\quad (60 \text{ s/min}) \\ &= 1.3 \times 10^3 \text{ J} \end{aligned}$$

- **b.** How many joules of thermal energy does the light bulb produce each minute?

$$\begin{aligned} E &= Pt \\ &= (0.78)(100.0 \text{ J/s})(1.0 \text{ min}) \\ &\quad (60.0 \text{ s/min}) \\ &= 4.7 \times 10^3 \text{ J} \end{aligned}$$