

# PQ 3b Resistance

Q and A

# Q1

- A car interior lamp with a resistance of 33 Ohm's is placed across a 12-V battery. What is the current through the circuit?

$$I = \frac{V}{R} = \frac{12 \text{ V}}{33 \ \Omega} = 0.36 \text{ A}$$

## Q2

- A motor with an operating resistance of 32 Ohm's is connected to a voltage source. The current in the circuit is 3.8 A. What is the voltage of the source?

$$V = IR = (3.8 \text{ A})(32 \ \Omega) = 1.2 \times 10^2 \text{ V}$$

## Q3

- A table lamp draws a current of 0.50 A when it is connected to a 120-V source.
- **a.** What is the resistance of the lamp?

$$R = \frac{V}{I} = \frac{120 \text{ V}}{0.50 \text{ A}} = 2.4 \times 10^2 \Omega$$

- **b.** What is the power consumption of the table lamp?

$$P = IV = (0.50 \text{ A})(120 \text{ V}) = 6.0 \times 10^1 \text{ W}$$

## Q4

- A 75-W table lamp is connected to 125 V.
- **a.** What is the current through the lamp?

$$I = \frac{P}{V} = \frac{75 \text{ W}}{125 \text{ V}} = 0.60 \text{ A}$$

- **b.** What is the resistance of the table lamp?

$$R = \frac{V}{I} = \frac{125 \text{ V}}{0.60 \text{ A}} = 2.1 \times 10^2 \text{ } \Omega$$

## Q5

- A 15 Ohm electric heater operates on a 120-V outlet.
- a. What is the current through the heater?

$$I = \frac{V}{R} = \frac{120 \text{ V}}{15 \Omega} = 8.0 \text{ A}$$

## Q6

- A 39 Ohm resistor is connected across a 45-V battery.
- a. What is the current in the circuit?

$$I = \frac{V}{R} = \frac{45 \text{ V}}{39 \Omega} = 1.2 \text{ A}$$

## Q7

- The resistance of an electric oven element at operating temperature is 11 Ohm's
- **a.** If 220 V are applied across it, what is the current through the stove element?

$$I = \frac{V}{R} = \frac{220 \text{ V}}{11 \Omega} = 2.0 \times 10^1 \text{ A}$$

## Q8

- A digital clock has a resistance of 12,000 Ohm's and is plugged into a 115-V outlet.
- a. How much current does it draw?

$$I = \frac{V}{R} = \frac{115 \text{ V}}{12,000 \Omega} = 9.6 \times 10^{-3} \text{ A}$$



