

PQ 3d

Questions

# Q1

A 110-volt toaster oven draws a current of 6 amps on its highest setting as it converts electrical energy into thermal energy. What is the toaster's maximum power rating?

## Q2

An electric iron operating at 120 volts draws 10 amperes of current. How much heat energy is delivered by the iron in 30 seconds?

Q3

One watt is equivalent to one

# Q4

A potential drop of 50 volts is measured across a 250-ohm resistor. What is the power developed in the resistor?

# Q5

A driving lamp fitted to a car is specified as a 100 W, 12.0 V lamp.

Calculate

- (a) the current flowing through the lamp, and
- (b) the resistance of the lamp.

# Q6

An electric motor found in a child's toy requires two 1.50 V dry cell batteries to be connected in series. If the motor draws a maximum current of 300 mA calculate

- (a) the resistance of the motor, and
- (b) the maximum power consumption of the toy.

# Q7

A Christmas tree is decorated by a string of 16 light globes which are connected in series to a mains outlet of 240 V. If the total power consumption is 24.0 W, calculate the

- (a) potential difference across each light globe, and
- (b) resistance of each light globe.

# Q8

Charles wishes to connect a number of 75.0 W, 240 V coloured party light globes around his patio. How many globes can he use without blowing a 10.0 A fuse when he turns the light globes on?



