

PQ 3e

Q and A

# Q1

There is a current of 40 mA in a lamp filament for 16 s. Calculate the quantity of charge that passes any fixed point in the circuit in this time.

$$Q = It$$

$$Q = 40 \times 10^{-3} \times 16$$

$$Q = 640 \times 10^{-3}$$

$$\text{Charge passing} = \underline{\underline{0.64 \text{ C}}}$$

## Q2

A flash of lightning lasts for 1 ms. The charge transferred between the cloud and the ground in this time is 5 C. Calculate the mean current in this flash of lightning.

$$Q = \bar{I}t$$

$$\bar{I} = Q/t$$

$$\bar{I} = 5/10^{-3}$$

$$\bar{I} = 5 \times 10^3$$

Current is  $5 \times 10^3$  A.

# Q3

The current in a circuit is  $2.5 \times 10^{-2}$  A. How long does it take for 500 C of charge to pass any given point in the circuit?

$$Q = It$$

$$t = Q/I$$

$$t = \frac{500}{2.5 \times 10^{-2}}$$

$$t = 2 \times 10^4$$

Time is  $2 \times 10^4$  s

# Q4

A resistor of value  $180\ \Omega$  has a current of  $68.0\ \text{mA}$  flowing through it. What is the p.d. across it?

$$V = IR$$

$$V = 0.068 \times 180$$

$$V = 12.24$$

P. d is 12.2V (12V)

# Q5

What current flows through a  $4.7 \text{ k}\Omega$  when the p.d across it is  $98.4 \text{ V}$ ?

$$V = IR$$

$$I = V/R$$

$$I = \frac{98.4}{4.7 \times 10^3}$$

$$I = 0.020936$$

Current is  $2.1 \times 10^{-2} \text{ A}$  ( $21 \text{ mA}$ )

# Q6

A p.d. of 450 V is placed across a resistor of 33.0 k $\Omega$ . Calculate the current flowing through it.

$$V = IR$$

$$\therefore I = \frac{V}{R}$$

$$\therefore I = \frac{450}{33.0 \times 10^3}$$

$$\therefore I = 0.01363636$$

Current is  $1.36 \times 10^{-2}$  (13.6 mA)

# Q7

The power dissipated by a 3.3 k $\Omega$  resistor is 250 mW. Find the p.d. across the resistor.

$$P = \frac{V^2}{R}$$

$$\therefore V^2 = PR$$

$$\therefore V^2 = 0.250 \times 3.3 \times 10^3$$

$$\therefore V^2 = 825$$

$$\therefore V = 28.7228 \quad \text{P.d is } \underline{\underline{28.7}} \quad (29V)$$

# Q8

A  $27 \Omega$  resistor has a current of  $0.573 \text{ A}$  flowing through it. Determine the power of the resistor.

$$P = I^2 R$$

$$P = 0.573^2 \times 27$$

$$P = 8.86488$$

Power is 8.86 W (8.9 W)

## Q9

A 60 W filament lamp is connected to the mains supply (230 V). What current flows in the filament?


$$P = IV$$
$$\therefore I = \frac{P}{V}$$
$$\therefore I = \frac{60}{230}$$
$$\therefore I = 0.2608696$$

Current is 0.26 A.


# Q10

Calculate the p.d. across the  $50\ \Omega$  load resistor in each of the following circuits.

(a)

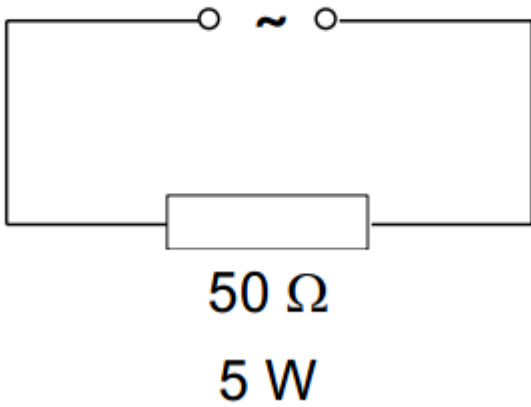

(b)

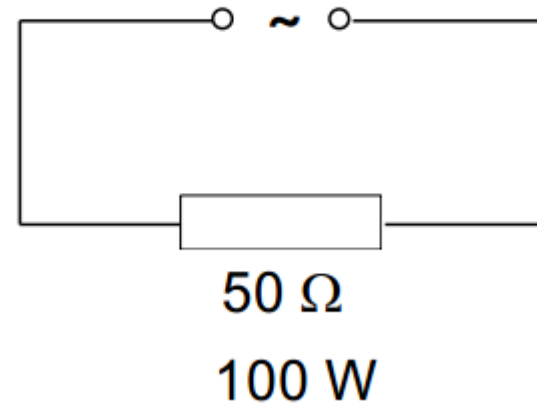

# Q10 continued

$$(a) \quad P = \frac{V^2}{R}$$

$$\therefore V^2 = PR$$

$$\therefore V^2 = 5 \times 50$$

$$\therefore V^2 = 250$$

$$\therefore V = 15.81139$$

P.d. is 16 V

$$(b) \quad P = \frac{V^2}{R}$$

$$\therefore V^2 = PR$$

$$\therefore V^2 = 50 \times 100$$

$$\therefore V^2 = 5000$$

$$\therefore V = 70.711$$

P.d. 70.7 V (71 V)